

Q. 1.

(10)

A 50-hp, 250-V 1200 r/min dc shunt motor with compensating windings has an armature resistance (including the brushes and interpoles) of  $0.06 \Omega$ . Its field circuit has a resistance  $R_F$  of  $25 \Omega$  with adjustable resistance  $R_{adj}$ , variable in  $0 \sim 100 \Omega$ . Which produces a no-load speed of 1200 r/min. There are 1200 turns per pole on the shunt field winding. The magnetization curve of this machine is shown in Fig. 1.

- For some load, when  $R_{adj} = 25 \Omega$ , the speed of the motor is 1250. Calculate the armature current  $I_A$ , converted power  $P_{conv}$  and induced torque.
- For the armature current calculated in (a), Find the range of speed achieved by this motor by field resistance control method.
- Calculate the total starting resistance and number of stages necessary if we want to limit the armature current between the value calculated in (a) and twice that.

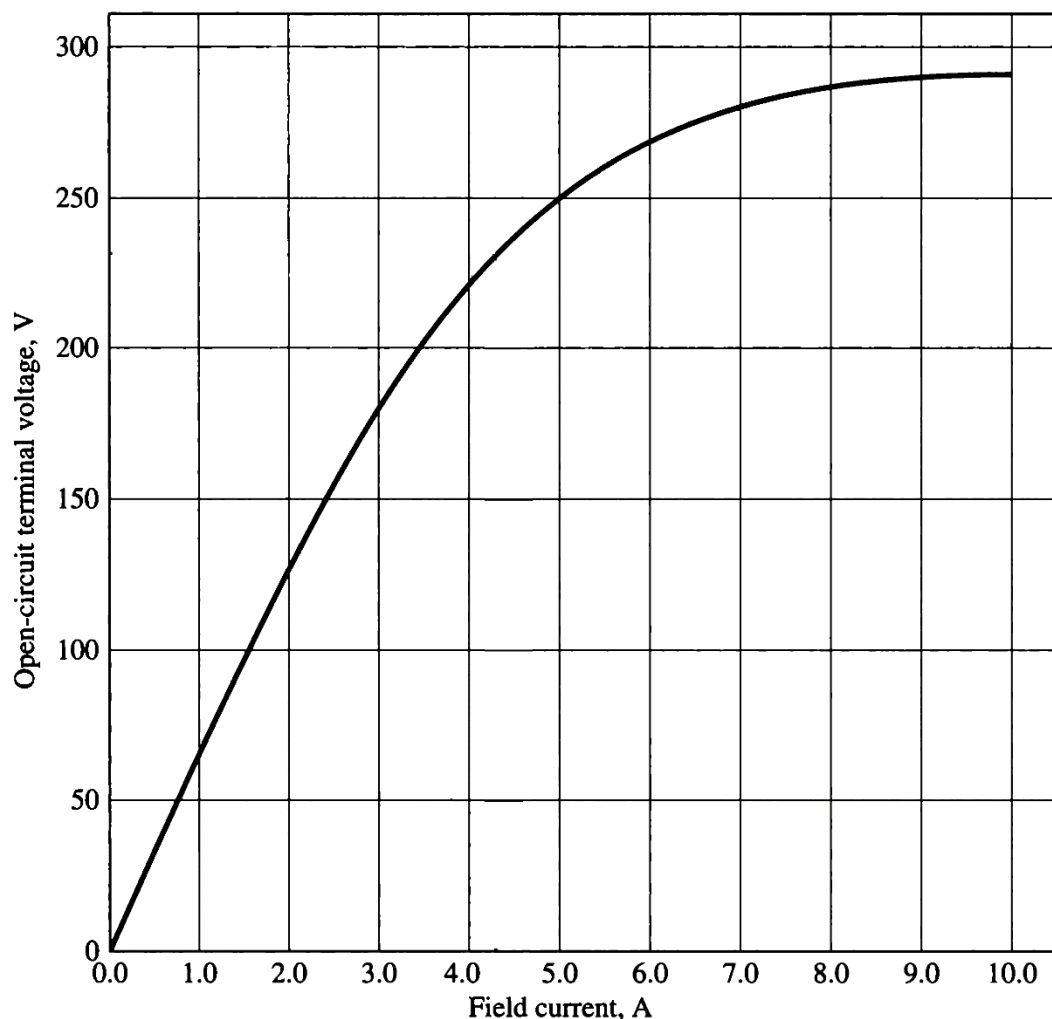


FIGURE 8-9

The magnetization curve of a typical 250-V dc motor, taken at a speed of 1200 r/min.

Q. 2 (05)

The motor described in Q. 1 is being used as a generator. If shaft speed is 1200 r/min,  $R_{adj} = 25 \Omega$ , then,

- (a) What is the no load voltage?
- (b) After some electrical load is connected, the terminal voltage drops to 200 V. What is the armature current?

Q. 3 (05)

How does the  $R_A$  control method affect the no-load speed of a separately excited dc motor? Explain with relevant curve/equation.